

CHOPPERS

Basic overview:

Chopper circuits are fundamental in power electronics for DC-DC voltage conversion.

Core Concepts:

- **What is a chopper?**

A chopper, also known as a DC-DC converter, is a switching circuit that converts a DC voltage to another DC voltage level, either higher or lower, using semiconductor switches.



- **What are the key components of a chopper circuit?**

A basic chopper circuit includes a semiconductor switch (e.g., BJT, MOSFET, IGBT), an inductor, and a diode.

- **How does a chopper operate?**

The switch is periodically switched on and off, controlling the voltage and current flow through the inductor and load. The average output voltage is controlled by varying the ON time (duty cycle) or switching frequency of the switch.

- **What is duty cycle?**

The duty cycle is the ratio of the ON time to the total period of the switching cycle. It directly affects the average output voltage.

Types of Choppers:

- **Step-down chopper:** Reduces the input voltage to a lower DC voltage.
- **Step-up chopper:** Increases the input voltage to a higher DC voltage.
- **Step-up/step-down chopper:** Can step up or step down the voltage depending on the duty cycle.

Control Strategies:

- **Constant frequency control:** The switching frequency is held constant, and the duty cycle is varied to control the output voltage.
- **Variable frequency control:** The switching frequency is varied, and the duty cycle is held constant or varied.
- **Pulse Width Modulation (PWM) control:** The ON time of the switch is modulated to control the output voltage.

Applications:

- **DC-DC converters in power supplies:** Used to step up or step down voltage for various electronic devices.
- **DC motor speed control:** Choppers are used to control the speed of DC motors by varying the voltage applied to the motor.
- **Battery chargers:** Choppers are used to charge batteries efficiently by controlling the charging voltage and current.

Other Important Questions:

- **What are the advantages of using a chopper?** Choppers offer advantages such as high efficiency, compactness, and flexibility in controlling voltage and current.

- **What are the limitations of choppers?** Choppers can have high switching losses and harmonics, especially at high frequencies.
- **What are some common switching devices used in choppers?** BJTs, MOSFETs, and IGBTs are commonly used.
- **What are the different types of commutation techniques used in choppers?** Forced commutation and load commutation are commonly used.

Example Questions and Answers:

- **Question:**

Explain the principle of operation of a step-down chopper.

- **Answer:** A step-down chopper reduces the input DC voltage by periodically switching a switch on and off. When the switch is ON, the inductor stores energy, and when it is OFF, the inductor releases energy back to the load, resulting in a lower average output voltage than the input voltage.

- **Question:**

How does duty cycle affect the output voltage of a chopper?

- **Answer:** The duty cycle, which is the ratio of the ON time to the total period, directly affects the average output voltage. A higher duty cycle results in a higher average output voltage.

- **Question:**

What are the advantages and disadvantages of using a GTO (Gate Turn-Off thyristor) in a chopper circuit?

- **Answer:** GTOs offer high switching speeds and can handle high currents, but they have relatively high turn-off losses compared to MOSFETs or IGBTs. Great! Here's the **complete, structured interview Q&A guide on choppers** in power electronics — with all **35 questions and their layman-friendly answers**. This covers everything from basic concepts to advanced technical topics, including **buck, boost, buck-boost, Cuk, SEPIC, bidirectional choppers**, and more.

Let us dive deep into the topic to develop an in-depth understanding :

SECTION 1: FUNDAMENTALS (BASIC LEVEL)

1. What is a chopper in power electronics?

A chopper is an electronic circuit that **controls DC voltage**. It does this by turning the power ON and OFF very fast, which changes how much average voltage the load receives. It's like a DC transformer.

2. Why are choppers used?

They help us **control or change DC voltage efficiently**, without wasting much energy.

They're used in:

- Electric vehicles
- DC motor drives
- Battery chargers
- Solar energy systems

3. What are the different types of DC-DC choppers?

The main types are:

- **Buck Converter** (Step-down)
- **Boost Converter** (Step-up)
- **Buck-Boost Converter** (Step-up/down with reversed polarity)
- **Cuk Converter**

- **SEPIC Converter**
- **Bidirectional Chopper**
- **Dual Converter**
- **Multiphase Converter**

4. What are the advantages of using a chopper?

- High efficiency
- Compact size
- Faster response
- Better control over output
- Works well with digital systems (PWM control)

5. How does a chopper differ from a linear regulator?

A chopper **switches ON and OFF** rapidly, saving power. A linear regulator **wastes extra voltage as heat**, making it less efficient.

6. What is PWM and how is it used in choppers?

Pulse Width Modulation (PWM) is a method to control how long the switch stays ON. By adjusting the ON time, we control the output voltage.

7. What is duty cycle and how does it affect output voltage?

Duty cycle is the ratio of ON time to total time.

For example, if the switch is ON 50% of the time, the duty cycle is 0.5.

In a buck converter:

$$V_{out} = D \times V_{in}$$

So, increasing duty cycle increases output voltage.

8. What is continuous and discontinuous conduction mode?

- **Continuous:** Current keeps flowing, even when the switch is OFF.
- **Discontinuous:** Current drops to zero for some time.
Continuous mode is smoother and better for steady loads.

9. What components make up a chopper circuit?

- **Switch** (MOSFET or IGBT): Turns power ON/OFF
- **Inductor**: Stores energy
- **Capacitor**: Smooths output voltage
- **Diode**: Allows one-way current
- **Controller**: Generates PWM signals

7. How are choppers classified based on quadrant operation?

Choppers can be classified based on voltage and current directions:

Class	Quadrant	V _o Sign	I _o Sign	Description
A	I	+	+	Motoring mode only
B	II	+	-	Regenerative braking
C	I & II	+	±	Two-quadrant chopper
D	I & IV	±	+	Bidirectional voltage
E	I to IV	±	±	Four-quadrant chopper

SECTION 2: BUCK (STEP-DOWN) CONVERTER

10. What is a Buck Converter and how does it work?

A Buck Converter **reduces the DC voltage**. It turns a switch ON and OFF rapidly. The longer it's ON (higher duty cycle), the higher the output — but it always stays **lower than the input**.

FORMULA:

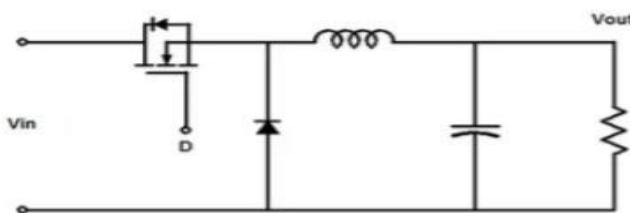


Figure 5 Buck Converter

$$V_{out} = D \cdot V_{in}$$

11. Where is a Buck Converter used?

- Phone and laptop chargers
- Electric vehicles (low-voltage logic control)
- LED dimming circuits
- DC motors requiring lower voltage

12. How does output voltage relate to duty cycle in a buck converter?

$$V_{out}=D \times V_{in}$$

If duty cycle is 0.4 and input is 24V, output = 9.6V.

13. What happens to current and voltage in a buck converter?

Voltage goes **down**, but current often goes **up** (to maintain power).

$$P=V \times I$$

14. How does load inductance affect buck chopper performance?

More inductance = smoother current

Too little inductance = noisy or pulsed current


SECTION 3: BOOST (STEP-UP) CONVERTER

15. What is a Boost Converter and how does it work?

A Boost Converter **increases DC voltage**. It stores energy in an inductor when the switch is ON and releases it when the switch is OFF, adding to the input voltage.

Formula:

$$V_{out} = \frac{V_{in}}{1 - D}$$

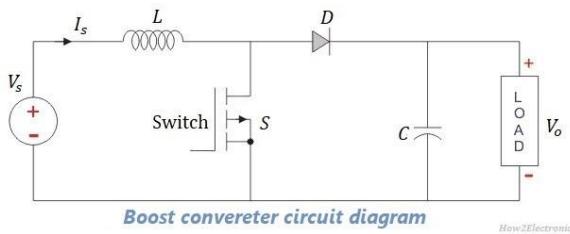

16. Where is a Boost Converter used?

- Solar panels (to boost low voltage)
- Electric vehicles
- Battery-powered devices needing higher voltage
- LED drivers

17. What are the challenges with Boost Converters?

- Output current is lower
- Voltage can spike if not controlled
- Needs good filtering to avoid ripple

18. How does the inductor function in a boost chopper?

It acts like a spring:

- **Stores energy** when switch is ON
- **Releases energy** when switch is OFF → boosts voltage


SECTION 4: BUCK-BOOST & OTHER CHOPPERS

19. What is a Buck-Boost Converter and where is it used?

It can **increase or decrease voltage**, and its output is **negative** (reversed polarity). Used when input voltage varies but fixed output is needed.

Formula:

$$V_o = \frac{-D}{1-D} V_s$$

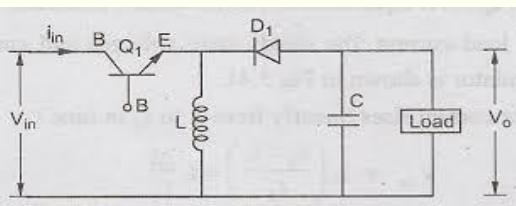

20. How is Buck-Boost different from Buck or Boost?

Converter	Output Voltage	Polarity
Buck	< Input	Same
Boost	> Input	Same
Buck-Boost	> or < Input	Reversed

21. What is a Cuk converter and how is it better?


A Cuk converter is like a Buck-Boost but with **smoother current** (less ripple) on both sides. Used in:

- Audio systems
- Solar inverters

Formula:

Output voltage to input voltage ratio for CUK Converter

$$\frac{V_o}{E} = \frac{D}{1-D}$$

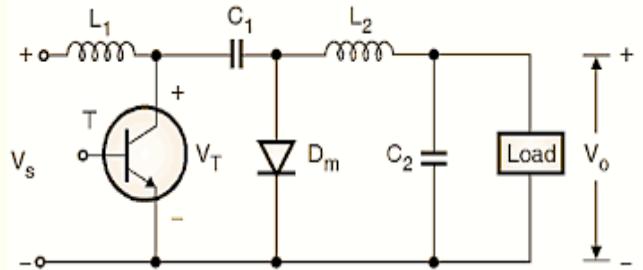

(not asked in interviews, just for extra knowledge)

22. What is a SEPIC converter and where is it used?

Like Cuk, but it gives **positive output polarity**. It can step up or down. Used in:

- Automotive electronics
- Battery-powered devices

23. What is a bidirectional chopper?

It allows power to **flow both ways** — useful in:

- Regenerative braking
- Charging/discharging batteries
- Energy storage systems

24. What is a dual converter and how does it relate to bidirectional choppers?

A **dual converter** uses two choppers — one for forward power and one for reverse. It's a type of **bidirectional chopper** used in motor drives.

SECTION 5: DESIGN & PROTECTION

25. What is the purpose of the freewheeling diode in choppers?

It gives a path for inductor current when the switch is OFF, preventing voltage spikes and protecting the switch.

26. How do you protect chopper circuits from voltage spikes?

- Use **snubber circuits**
- Add **freewheeling diodes**
- Include **TVS diodes or MOVs**

27. How do filters help in choppers?

Filters (capacitors + inductors) **smooth out the voltage and current**, reducing noise (ripple).

28. What causes switching losses in a chopper circuit?

Losses occur during the brief time when voltage and current **overlap** as the switch turns ON or OFF. This causes heat.

29. What is the difference between hard switching and soft switching?

- **Hard switching:** High losses and stress on the switch
- **Soft switching:** Turns switch ON/OFF when voltage/current is zero → less heat and higher efficiency

22. What are snubber circuits and why are they used?

Snubbers protect switching devices from voltage spikes by absorbing energy from inductive

components.

23. How do freewheeling diodes work in choppers?

They provide a path for inductor current when the main switch is OFF, preventing high voltage across the switch.

SECTION 6: ADVANCED CONTROL & APPLICATIONS

30. How does electromagnetic interference (EMI) affect chopper circuits?

Fast switching creates EMI, which can disturb nearby devices. It's controlled using:

- Shielding
- Filters
- Proper PCB layout

31. What is the role of digital controllers (MCUs, DSPs) in choppers?

They generate precise PWM signals and use feedback to adjust output voltage quickly and accurately.

32. What is closed-loop control in choppers?

It uses a **feedback system** to constantly monitor and correct the output voltage, keeping it stable.

33. Why are MOSFETs preferred in high-frequency choppers?

MOSFETs switch **faster** and have **low losses**, making them ideal for high-speed chopper circuits.

34. What is isolation in DC-DC converters and why is it important?

Isolation separates input and output circuits to:

- Protect the user
- Prevent faults
- Break ground loops
Used in **medical and industrial** systems

35. How do choppers handle rapid load changes or dynamic loads?

Using:

- Fast PWM control
- Feedback loops
- Larger capacitors
They adjust duty cycle in real time to keep voltage stable.
-

26. What is ripple and how is it minimized?

Ripple is the unwanted variation in output voltage.

Minimized using **output capacitors** and **inductors**.

39. What is a practical limitation of very high switching frequency?

It increases:

- Switching losses
- EMI
- Complexity of driver circuitry

40. How do choppers behave under short-circuit conditions?

Excess current may damage the switch — protection via:

- Current sensing
- Fast shutdown
- Fuses or crowbars

SECTION 7: APPLICATION BASED QUESTIONS

1. How are choppers used in electric vehicles (EVs)?

Answer:

In EVs, choppers control the speed and torque of DC motors by varying the DC voltage supplied to them. For example:

- During acceleration, the chopper increases the duty cycle to supply more voltage.
- During regenerative braking, Class B or Bidirectional choppers redirect power from the motor back to the battery.

2. Can you explain how choppers are used in solar power systems?

Answer:

Choppers like boost converters are used in solar charge controllers to step up the low voltage from solar panels to match the battery voltage. They also implement MPPT (Maximum Power Point Tracking) to extract maximum power from the solar panels.

3. Where are choppers used in public transportation?

Answer:

In electric trains, trams, and metros, choppers regulate the DC voltage supplied to traction motors. This helps in smooth speed control, energy-efficient operation, and regenerative braking during deceleration.

4. Are choppers used in mobile phone chargers or power banks?

Answer:

Yes. Buck converters are used to step down the 5V or higher USB supply voltage to safely charge mobile batteries (usually ~3.7V). They ensure high efficiency and reduce heat generation.

5. How do choppers help in home appliances?

Answer:

Devices like cordless drills, fans, and mixers use choppers to control motor speed. Instead of using bulky transformers or resistive control, a chopper efficiently regulates the DC motor voltage.

6. What role do choppers play in UPS (Uninterruptible Power Supply) systems?

Answer:

In UPS systems, buck-boost converters ensure a constant output voltage despite fluctuations in input supply or battery discharge level. They stabilize the DC bus before it's inverted to AC.

7. Can you give an example of chopper use in robotics?

Answer:

In robotic arms and mobile robots, choppers precisely control the speed and direction of DC motors to ensure accurate movement. Bidirectional choppers are used for motion in both directions.

8. Are choppers used in aerospace or satellite systems?

Answer:

Yes. Space applications use isolated DC-DC converters (based on chopper principles) for power distribution to sensitive electronics. Efficiency and weight reduction are critical here.

9. How are choppers useful in smart grid or battery management systems (BMS)?

Answer:

Choppers help in balancing cells during charging/discharging, managing current flow direction, and protecting batteries. They are also used to control energy flow in DC microgrids.

10. Can you relate chopper usage in daily consumer electronics?

Answer:

Yes, devices like LED drivers, laptops, and TV power supplies use buck/buck-boost converters for internal DC voltage regulation. This ensures that each component gets its required voltage efficiently.

INTERVIEW SATHI